

DLD Target Guide

Final Examination Preparation

A curated study roadmap based on past trends and course outlines.

Note from the Compiler

I have carefully analyzed past examination trends, the official course syllabus, and insights from previous batches to organize this preparation guide. My goal is to help everyone streamline their studies and understand the expected paper pattern. Please note that this is a personal roadmap, not an official paper. Use it to structure your preparation effectively.

How To Use This Target Paper

- ▶ **Do not memorize blindly.** Understand the underlying logic.
- ▶ **Focus heavily on logic diagrams.** They carry the most weight.
- ▶ **Solve at least 2 practice questions per topic** to build muscle memory.
- ▶ **Use this guide as a preparation roadmap**, not as a replacement for core concepts.

Expected Exam Structure

- ▶ **MCQs Section:** Will prominently feature *Number System Conversions* (all bases: Binary ↔ Octal ↔ Decimal ↔ Hexadecimal). There will likely be no long theoretical or practical questions on conversions in the subjective paper.
- ▶ **Subjective Section Format:** The main paper is expected to have **7 Questions**, out of which **6 must be attempted**.
- ▶ **Marks & Weightage:** All questions will carry equal marks. There is no concept of separate "short" or "long" questions.
- ▶ **Mixed Question Parts:** Every question will typically have **2 parts (e.g., a and b)**. These parts will tightly mix practical circuit-solving with theoretical concepts.

Complete Course Outline Reference

Ensure no topic from this official outline is left completely untouched:

Topic Area	Sub-topics Included
Fundamentals	Number System & Conversions, Digital Circuits
Logic Gates	Basic Gates, Universal Gates, Logic Diagrams
Boolean Logic	Boolean Algebra, Laws, SOP/POS, K-Maps
Combinational	Adders (Half/Full), Subtractors, Encoder/Decoder, MUX/DEMUX
Sequential	Synchronous/Asynchronous, Latches, Flip Flops (SR, JK, D), Counters
System Components	Memory (RAM/ROM), Registers, Clocks, 7-Segment Display

Part 1: Analytical & Diagrammatic Questions

These are the core solving questions. They will be mixed and matched with the theory questions below to form the (a) and (b) parts of the main paper.

Q1. Boolean Expression Simplification

- ▶ **Format:** You will be given complex Boolean expressions.
- ▶ **Task:** Prove or simplify them step-by-step using standard Boolean laws and theorems.

Q2. Truth Table to Equation

- ▶ **Format:** A completely filled truth table will be provided.
- ▶ **Task:** Extract and write the equivalent SOP (Sum of Products) or POS (Product of Sums) equation directly from the table outputs.

Q3. Adder / Subtractor Design

- ▶ **Format:** 1 guaranteed question from Half/Full Adder or Half/Full Subtractor. (**High chance of Full Adder**).
- ▶ **Task:** Write the definition, draw the truth table, formulate the Boolean expressions for Sum/Carry (or Difference/Borrow), and draw the final logic diagram.

Q4. Equation to Logic Diagram

- ▶ **Format:** A Boolean expression will be given.
- ▶ **Task:** Construct its Truth Table and map out the equivalent Logic Diagram using standard gates.

Q5. Logic Diagram to Equation

- ▶ **Format:** A logic circuit diagram will be printed on the exam paper.
- ▶ **Task:** Trace the logic gates from input to output and write the final Boolean expression for the circuit.

Q6. De Morgan's Law

- ▶ **Format:** 1 dedicated question on this critical theorem.
- ▶ **Task:** State and mathematically prove De Morgan's theorems. You must include the truth tables and logic diagrams in your proof to secure full marks.

Q7. Universal Gates Implementation

- ▶ **Format:** 1 specific gate implementation question.
- ▶ **Task:** Implement all the basic logic gates (AND, OR, NOT) using **only NAND gates** or **only NOR gates**.

Q8. Karnaugh Map (K-Map) Minimization

- ▶ **Format:** 1 highly important minimization question (likely 3-variable or 4-variable).
- ▶ **Task:** Minimize a given SOP (Sum of Products) equation using a K-map and group the terms correctly.

Q9. Latches & Flip Flops Conversion

- ▶ **Format:** 1 question focusing on Sequential Logic (SR Latch, or SR, JK, D, T Flip Flops).
- ▶ **Task:** Explain how to construct one from another (e.g., Construct a JK Flip-Flop using an SR Flip-Flop). Include excitation tables, truth tables, and logic diagrams.

Part 2: Theory & Conceptual Questions

These descriptive questions will be paired with the analytical questions above. Keep answers concise but comprehensive.

Q10. Digital Circuits Overview

- ▶ **Task:** Define what a digital circuit is, its advantages over analog, and explain its core components.

Q11. Critical Differences

- ▶ **Format:** 1 guaranteed question asking to differentiate between two core concepts.
- ▶ **Task:** Give 4 to 5 clear, tabular differences for any of the following pairs:
 - Synchronous vs. Asynchronous Circuits
 - Combinational vs. Sequential Circuits
 - Latches vs. Flip Flops
 - RAM vs. ROM
 - Truth Table vs. Excitation Table
 - SOP (Sum of Products) vs. POS (Product of Sums)
 - NAND Gate vs. NOR Gate

Q12. Registers

- ▶ **Task:** What is a register? Explain the different types of shift registers (SISO, SIPO, PISO, PIPO) briefly.

Q13. Memory & Types

- ▶ **Task:** Define memory architecture. Differentiate between primary and secondary memory. Define RAM and ROM, and explain their volatile/non-volatile nature and sub-types (SRAM, DRAM, PROM, EEPROM).

Q14. Clock Signals

- ▶ **Task:** What is a clock signal? Explain its necessity in sequential logic and the types of triggering (Edge-triggered vs. Level-triggered).

Q15. Standard Form Conversions

- ▶ **Task:** Convert a given standard SOP expression to its canonical POS form, and vice versa.

Q16. 7-Segment Display

- ▶ **Task:** Draw the block diagram of a BCD to 7-Segment Display decoder and formulate its truth table for a Common Cathode or Common Anode configuration.

Priority Preparation Strategy

Mastery Checklist (Study in this order)

1. **Number System & Boolean Laws:** The absolute foundation. Secure MCQ marks and basic expression simplification skills first.
2. **K-Map Minimization:** Highly predictable and carries solid marks. Learn to group pairs, quads, and octets flawlessly.
3. **Adder / Subtractor Design:** Memorize the Full Adder logic diagram and truth table perfectly. It is a staple question.
4. **Logic Gates & Universal Gates:** Be able to draw and convert any gate instantly using NAND/NOR configurations.
5. **Flip Flops & Latches:** Focus heavily on understanding the differences in their Truth Tables and how to design one from another.
6. **Differences Cheat Sheet:** Create a quick 2-column reference sheet for all the "Differences" listed in Q11.
7. **Memory & Registers:** Leave this for last. Memorize the definitions and types for the theoretical parts of the paper.

Prepared & Compiled by

Shaikh Mahad

BSSE Student

[LinkedIn](#)

[GitHub](#)

[Join The UBIT Hub](#)